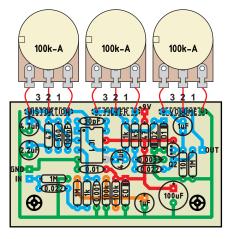
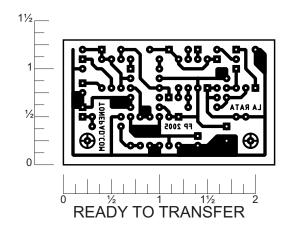


Build the RAT distortion on this layout. This is the original RAT circuit. Off board components except for the potentiometers are not shown on the layout. Trademarks remain property of their owners.



LAYOUT



Common parts

Resistors	Capacitors	Transistors &ICs
2 - 47	1 - 30 pF	1 - 2N5458
1 - 560	1 - 100 pF	IC1 - LM308
2 - 1k	1 - 0.001 µF	
1 - 1k5 (1.5k)	1 - 0.0033 µF	Diodes
1 - 10k ` ′	1 - 0.01 μF [˙]	2 - 1N914
2 - 100k	2 - 0.022 µF	1 - 1N4002
3 - 1M	2 - 1 µF .	
	1 - 2.2 μF	
Pots	2 - 4.7 µF	
3 - 100k Log.	1 - 100 µF	

Layout and presentation by Francisco Peña 2001-2005®. All rights reserved. Authorization for personal use only, any commercial use is forbidden. Permission for posting/serving limited to http://www.tonepad.com
Permission refused for posting from other sites.

